

Introduction to Physical Science

Electric Circuits

Presented by Robert Wagner

Types of Circuits

- Circuits will generally have multiple components (resistors)
- Two basic combinations
 - Series
 - Parallel

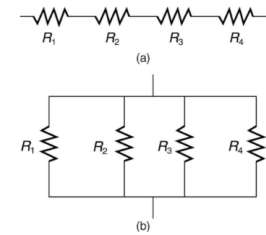


Image Credit: OpenStax College Physics - Figure 21.2 CC BY 4.0

Resistors in Series

- Resistors are in series when the current must flow through each resistor in turn
- Current is the same through each resistor
- The total resistance is the sum of the individual resistances

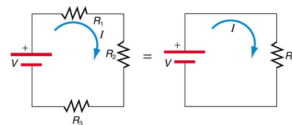


Figure 21.3 Three resistors connected in series to a battery (left) and the equivalent single or series resistance (right).

Image Credit: OpenStax College Physics - Figure 21.3 CC BY 4.0

Example

- A battery with voltage 12.0 V, is applied through three resistances (in series):

What are the total resistance, current and total power dissipated.

- Draw a sketch (if applicable)
- Identify known values
- Identify equation
- Enter values in the equation and solve

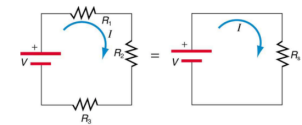


Figure 21.3 Three resistors connected in series to a battery (left) and the equivalent single or series resistance (right).

Image Credit: OpenStax College Physics - Figure 21.3 CC BY 4.0

Example

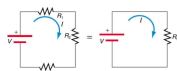


Figure 21.3 Three resistors connected in series to a battery (left) and the equivalent single or series resistance (right).

- A battery with voltage 12.0 V, is applied through three resistances (in series):

What are the total resistance, current and total power dissipated.

- Draw a sketch (if applicable)
- Identify known values
- Identify equation
- Enter values in the equation and solve

$$V = 12.0 \text{ V}; R_1 = 1.00\Omega, R_2 = 6.00\Omega, R_3 = 13.0\Omega$$

$$R_s = R_1 + R_2 + R_3$$

$$R_s = 1.00\Omega + 6.00\Omega + 13.0\Omega = 20.0\Omega$$

$$I = \frac{V}{R_s} = \frac{12.0 \text{ V}}{20.0 \Omega} = 0.600 \text{ A}$$

$$P = IV = (0.600 \text{ A})(12.0 \text{ V}) = 7.20 \text{ W}$$

Image Credit: OpenStax College Physics - Figure 21.3 CC BY 4.0

Example

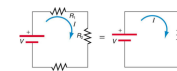


Figure 21.3 Three resistors connected in series to a battery (left) and the equivalent single or series resistance (right).

- A battery with voltage 12.0 V, is applied through three resistances (in series):

What is the voltage drop across each resistor?

- Draw a sketch (if applicable)
- Identify known values
- Identify equation
- Enter values in the equation and solve

$$V = 12.0 \text{ V}; R_1 = 1.00\Omega, R_2 = 6.00\Omega, R_3 = 13.0\Omega$$

$$V_1 = IR_1$$

$$V_1 = (0.600 \text{ A})(1.0 \Omega) = 0.600 \text{ V}$$

$$V_2 = IR_2$$

$$V_2 = (0.600 \text{ A})(6.0 \Omega) = 3.60 \text{ V}$$

$$V_3 = IR_3$$

$$V_3 = (0.600 \text{ A})(13.0 \Omega) = 7.80 \text{ V}$$

$$V_1 + V_2 + V_3 = 7.80 \text{ V} + 3.60 \text{ V} + 0.600 \text{ V} = 12.0 \text{ V}$$

Image Credit: OpenStax College Physics - Figure 21.3 CC BY 4.0

Resistors in Parallel

- In a parallel circuit, the current will be split among multiple resistors.
- Total resistance is the sum of the inverse of each resistance
-
- The total resistance will be less than all of the individual resistances

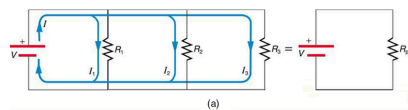


Image Credit: OpenStax College Physics - Figure 21.4a CC BY 4.0

Example

- A battery with voltage 12.0 V, is applied through three resistances (in parallel):

What are the total resistance, current and total power dissipated.

- Draw a sketch (if applicable)
- Identify known values
- Identify equation
- Enter values in the equation and solve


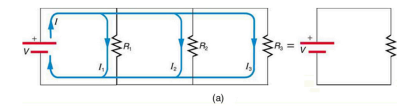


Image Credit: OpenStax College Physics - Figure 21.4a CC BY 4.0

Example

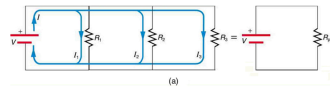

- A battery with voltage 12.0 V, is applied through three resistances (in parallel):

What are the total resistance, total current and total power dissipated.

- Draw a sketch (if applicable)
- Identify known values
- Identify equation
- Enter values in the equation and solve

$$V = 12.0 \text{ V}; R_1 = 1.00\Omega, R_2 = 6.00\Omega, R_3 = 13.0\Omega$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$


$$\frac{1}{R_p} = \frac{1}{1.00\Omega} + \frac{1}{6.00\Omega} + \frac{1}{13.0\Omega}$$

$$\frac{1}{R_p} = (1 + 0.167 + 0.0769) \frac{1}{\Omega}$$

$$\frac{1}{R_p} = 1.2439 \frac{1}{\Omega} \text{ or, } R_p = 0.804 \Omega$$

Image Credit: OpenStax College Physics - Figure 21.4a CC BY 4.0

Example

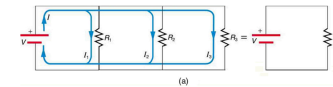

- A battery with voltage 12.0 V, is applied through three resistances (in parallel):

What are the total resistance, total current and total power dissipated.

- Draw a sketch (if applicable)
- Identify known values
- Identify equation
- Enter values in the equation and solve

$$V = 12.0 \text{ V}; R_1 = 1.00\Omega, R_2 = 6.00\Omega, R_3 = 13.0\Omega$$


$$R_p = 0.804 \Omega$$

$$I = \frac{V}{R_p} = \frac{12.0 \text{ V}}{0.804 \Omega} = 14.9 \text{ A}$$

$$P = IV = (14.9 \text{ A})(12.0 \text{ V}) = 179 \text{ W}$$

Image Credit: OpenStax College Physics - Figure 21.4a CC BY 4.0

Example

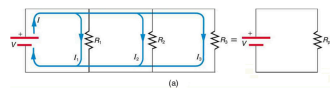

- A battery with voltage 12.0 V, is applied through three resistances (in parallel):

What is the current through each resistor?

- Draw a sketch (if applicable)
- Identify known values
- Identify equation
- Enter values in the equation and solve

$$V = 12.0 \text{ V}; R_1 = 1.00\Omega, R_2 = 6.00\Omega, R_3 = 13.0\Omega$$

$$I_1 = \frac{V}{R_1} = \frac{12.0 \text{ V}}{1.00 \Omega} = 12.0 \text{ A}$$

$$I_2 = \frac{V}{R_2} = \frac{12.0 \text{ V}}{6.00 \Omega} = 2.0 \text{ A}$$

$$I_3 = \frac{V}{R_3} = \frac{12.0 \text{ V}}{13.0 \Omega} = 0.92 \text{ A}$$

$$I_1 + I_2 + I_3 = 12.0 \text{ A} + 2.0 \text{ A} + 0.92 \text{ A}$$

$$I_1 + I_2 + I_3 = 14.92 \text{ A}$$

Image Credit: OpenStax College Physics - Figure 21.4a CC BY 4.0

Combination Circuits

- We often have more complex circuits involving both series and parallel components.
- We can reduce these to a single equivalent resistance

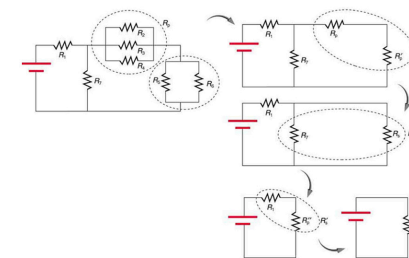


Image Credit: OpenStax College Physics - Figure 21.5 CC BY 4.0

Example

- For the circuit shown, find the total resistance, voltage drop across R_1 , current through R_2 , and power dissipated by R_2 .

- Draw a sketch (if applicable)
- Identify known values
- Identify equation
- Enter values in the equation and solve


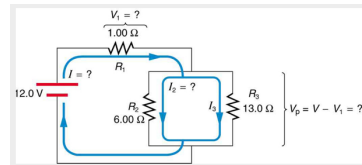


Image Credit: OpenStax College Physics - Figure 21.6 CC BY 4.0

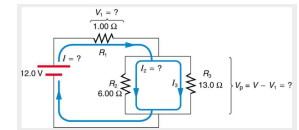Example

- For the circuit shown, find the total resistance, voltage drop across R_1 , current through R_2 , and power dissipated by R_2 .

- Draw a sketch (if applicable)
- Identify known values
- Identify equation
- Enter values in the equation and solve



$$\frac{1}{R_p} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{6.00 \Omega} + \frac{1}{13.0 \Omega}$$

$$\frac{1}{R_p} = 0.2436 \frac{1}{\Omega}$$

$$R_p = 4.11 \Omega$$


$$R_{tot} = R_1 + R_p = 1.00 \Omega + 4.11 \Omega = 5.11 \Omega$$

Image Credit: OpenStax College Physics - Figure 21.6 CC BY 4.0

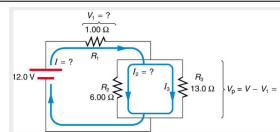Example

- For the circuit shown, find the total resistance, voltage drop across R_1 , current through R_2 , and power dissipated by R_2 .

- Draw a sketch (if applicable)
- Identify known values
- Identify equation
- Enter values in the equation and solve



$$I = \frac{V}{R_{tot}} = \frac{12.0 V}{5.11 \Omega} = 2.35 A$$

$$V_1 = IR_1$$

$$V_1 = (2.35 A)(1.00 \Omega) = 2.35 V$$

$$V_p = V - V_1 = 12.0 V - 2.35 V = 9.65 V$$

$$I_2 = \frac{V_p}{R_2} = \frac{9.65 V}{6.00 \Omega} = 1.61 A$$

$$P_2 = (I_2)^2 R_2 = (1.61 A)^2 (6.00 \Omega) = 15.5 W$$

Image Credit: OpenStax College Physics - Figure 21.6 CC BY 4.0

Problem Solving Strategies

- Draw a circuit diagram - label all resistors and voltage sources - this identifies your known values
- Identify unknowns
- Determine if the resistors are in series, parallel or a combination
- Reduce the problem in to steps considering how to handle series and parallel components
- Check to make sure answers are reasonable

Summary

- Electrical Circuits can involve resistors in series, parallel, or a combination of these two
- Resistors in series add directly and resistors in parallel add inversely
- Combination circuits are more complex and include both series and parallel components