

$$I_2 = \frac{V}{R_2} = \frac{12.0 \text{ V}}{6.00 \, \Omega} = 2.0 \text{ A}$$