

$$I_3 = \frac{V}{R_3} = \frac{12.0 \text{ V}}{13.00 \text{ }\Omega} = 0.92 \text{ A}$$