

$$P_2 = I_2^2 R_2 = (1.61 A)^2 (6.00 \Omega) = 15.5 W$$