

$$I_2 = \frac{V_p}{R_2} = \frac{9.65 \text{ V}}{6.00 \text{ }\Omega} = 1.61 \text{ A}$$