

$$I_1 = \frac{V}{R_1} = \frac{12.0 \text{ V}}{1.00 \text{ }\Omega} = 12.0 \text{ A}$$