

$$\frac{1}{R_p} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{6.00\,\Omega} + \frac{1}{13.0\,\Omega}$$