

$$\frac{1}{R_p} = \frac{1}{1.00\Omega} + \frac{1}{6.00\Omega} + \frac{1}{13.0\Omega}$$